


CIRCUIT FORMS DIVIDE BY 1.5 COUNTER

- Two inexpensive ICs divide a TTL clock signal by 1.5.
- By following the circuit with another flip/flop, you could also generate a divide by three function.

NOTE:

THIS CIRCUIT MAY NOT ALWAYS WORK AT HIGH CLOCK SPEEDS
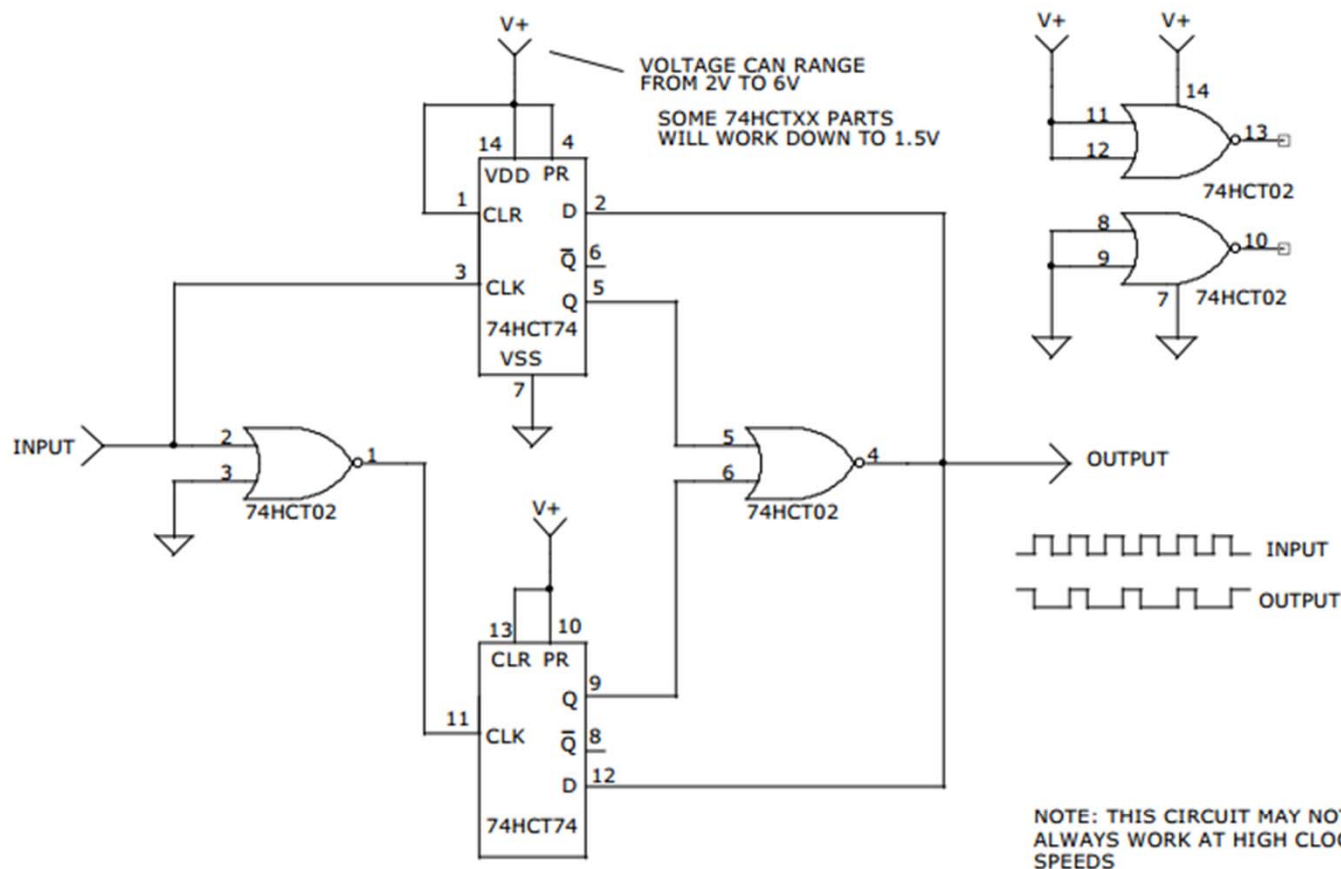
<http://www.discovercircuits.com/DJ-Circuits/divider1.htm>




DIVIDE BY 1.5 COUNTER

DRAWN BY: DAVE JOHNSON


DAVID JOHNSON AND ASSOCIATES		
DIVIDE BY 1.5 COUNTER		
Size A	Document Number DIVIDER1.DSN	2 Rev A
Date: Thursday, July 06, 2000	Sheet 1 of 1	

22/11/14

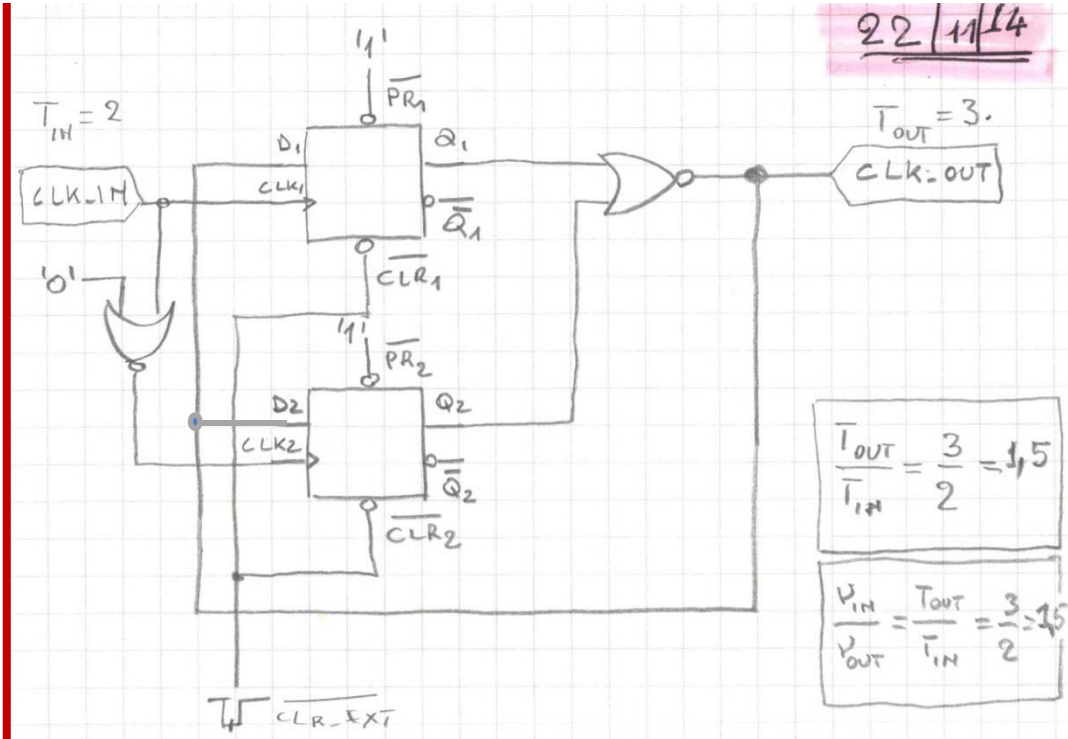


$$\frac{T_{OUT}}{T_{IN}} = \frac{3}{2} = 1.5$$

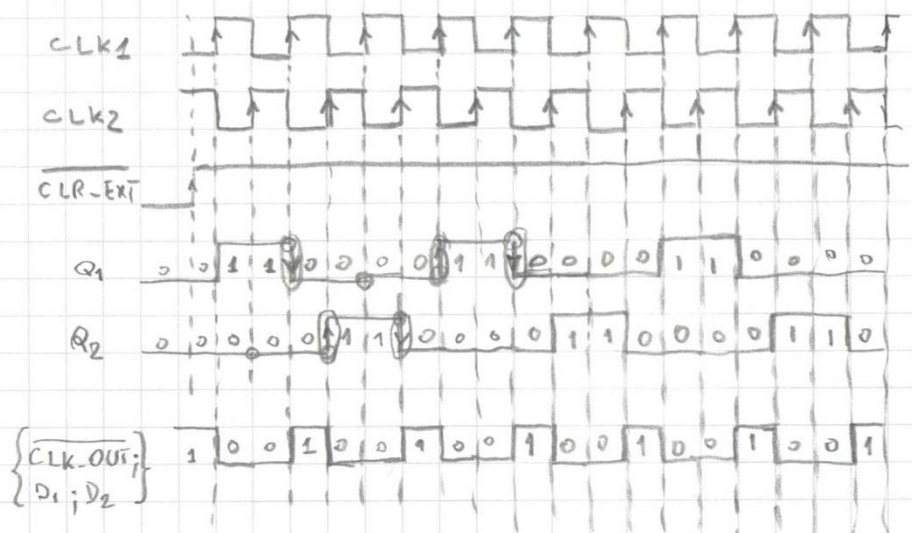
$$\frac{V_{IN}}{V_{OUT}} = \frac{T_{OUT}}{T_{IN}} = \frac{3}{2} = 1.5$$


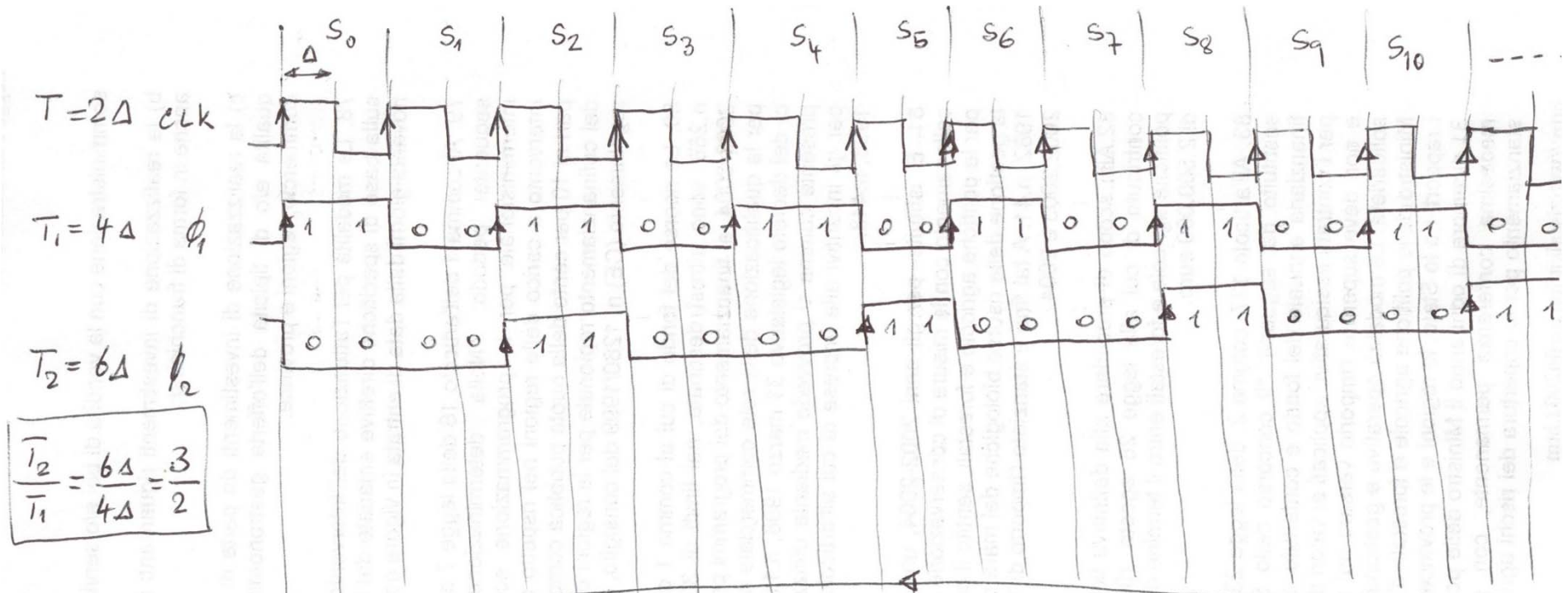
<http://www.discovercircuits.com/DJ-Circuits-divider1.htm>


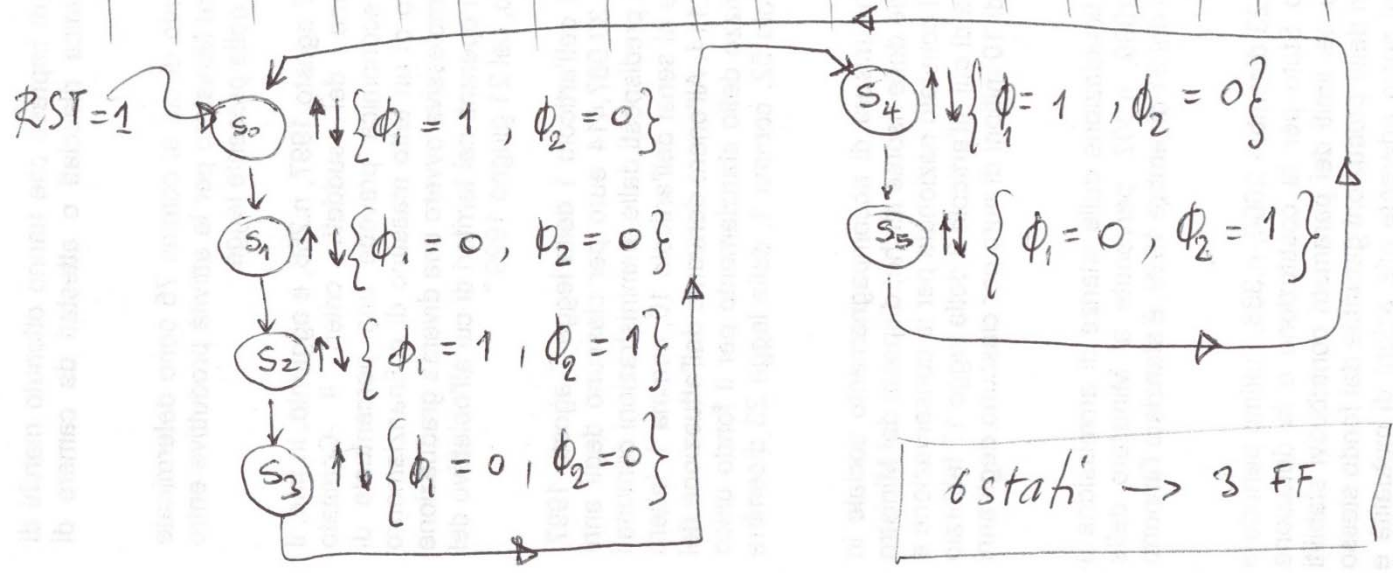
$$\frac{\overline{I_2}}{T_1} = \frac{6\Delta}{4\Delta} = \frac{3}{2}$$



@ t_n			@ t_{n+1}			@ t_n			@ t_n		
Q^A	Q^B	Q^C	Q^A	Q^B	Q^C	ϕ_1	ϕ_2	D^A	D^B	D^C	
0	0	0	0	0	1	1	0	0	0	1	
0	0	1	0	1	0	0	0	0	1	0	
0	1	0	0	1	1	1	1	0	1	1	
0	1	1	1	0	0	0	0	1	0	0	
1	0	0	1	0	1	1	0	1	0	1	
1	0	1	0	0	0	0	1	0	0	0	
1	1	0	x	x	x	x	x	x	x	x	
1	1	1	x	x	x	x	x	x	x	x	

Q^A	Q^B	Q^C	0	1
00			1	0
01			1	0
11			x	x
10			1	0

$\phi^1 = \bar{Q}^C$

Q^A	Q^B	Q^C	0	1
00			0	0
01			1	0
11			x	x
10			0	1

$\phi^2 = \bar{Q}^B \cdot \bar{Q}^C + Q^A \cdot Q^C$

Q^A	Q^B	Q^C	0	1
00			0	0
01			0	1
11			x	x
10			1	0


$D^A = Q^A \cdot \bar{Q}^C + Q^B \cdot Q^C$


Q^A	Q^B	Q^C	0	1
00			0	1
01			1	0
11			x	x
10			0	0

$D^B = Q^B \cdot \bar{Q}^C + \bar{Q}^A \cdot \bar{Q}^B \cdot Q^C$

Q^A	Q^B	Q^C	0	1
00			1	0
01			1	0
11			x	x
10			1	0

$D^C = \bar{Q}^C$

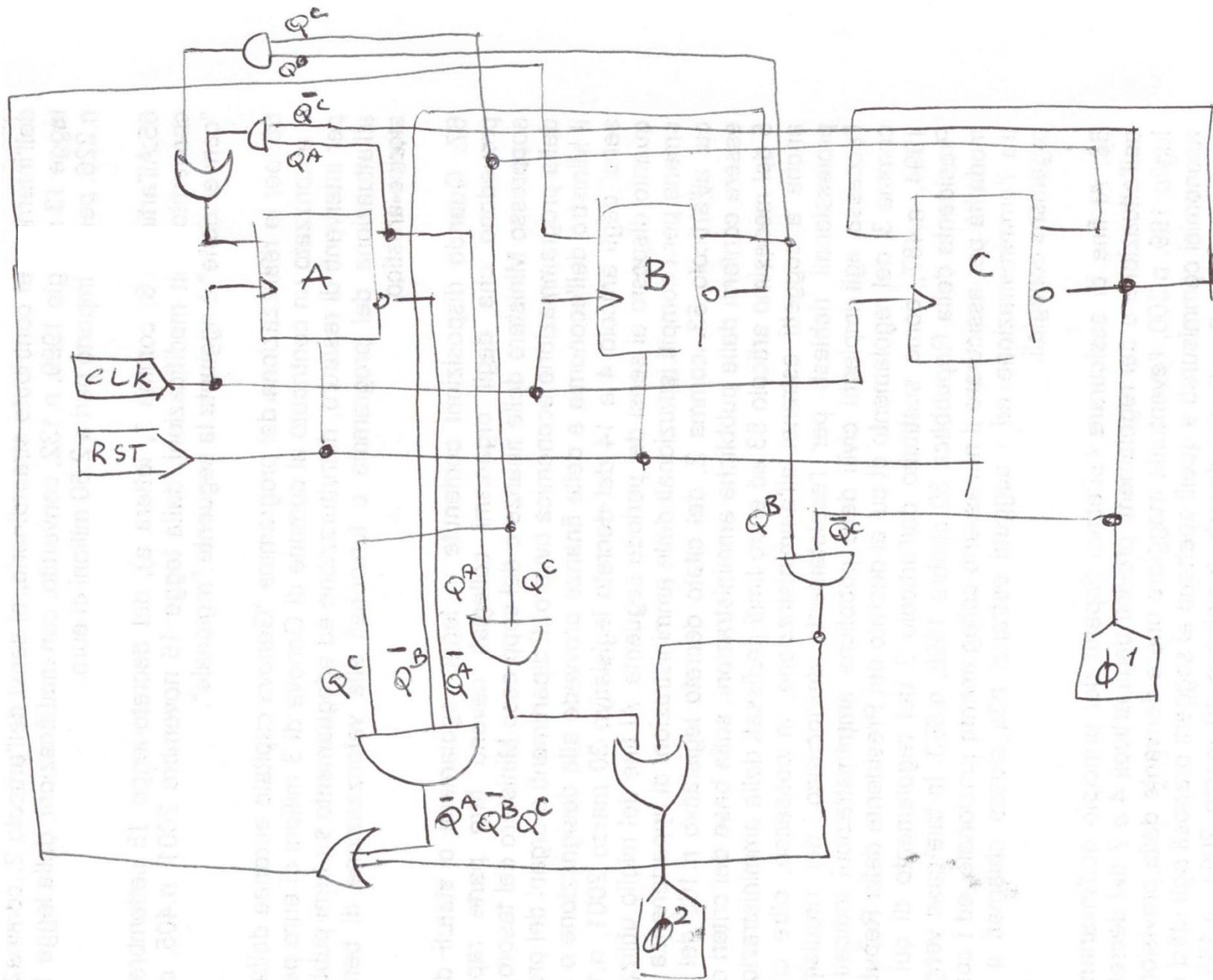


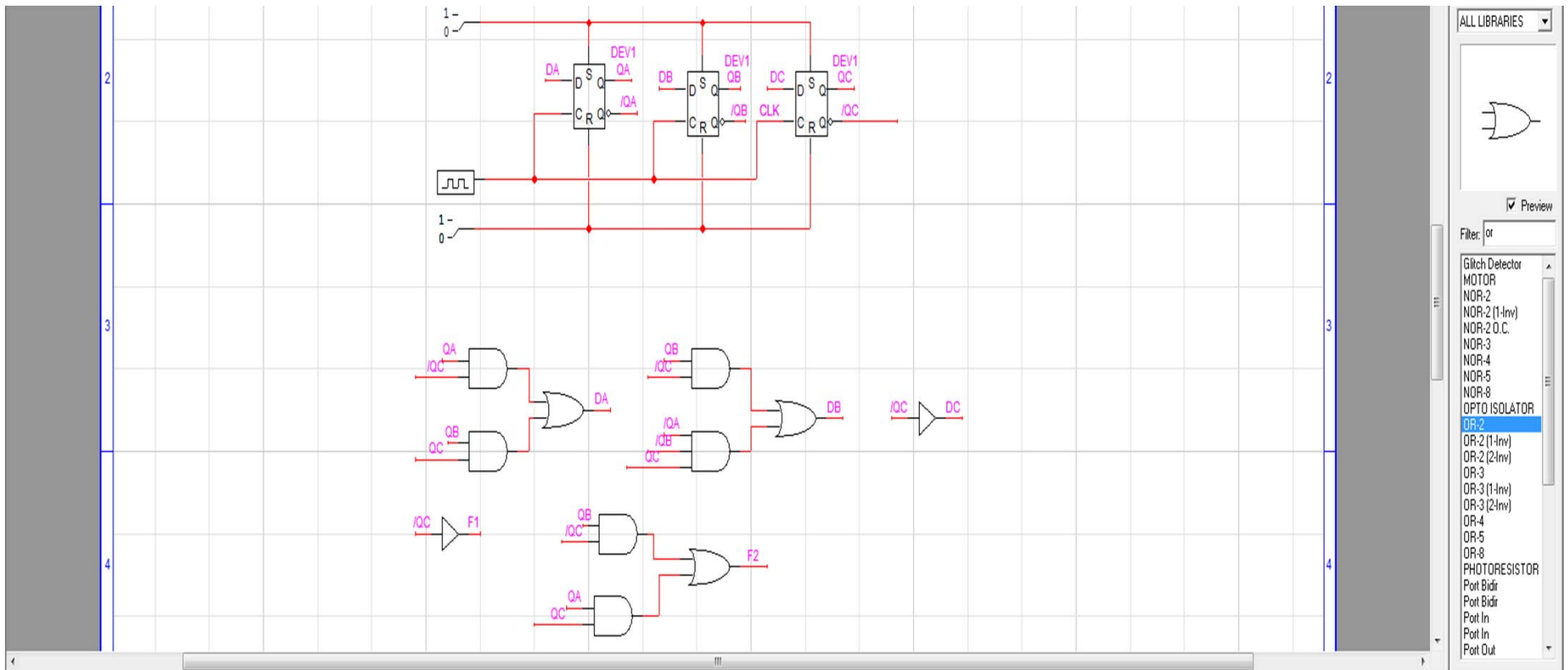

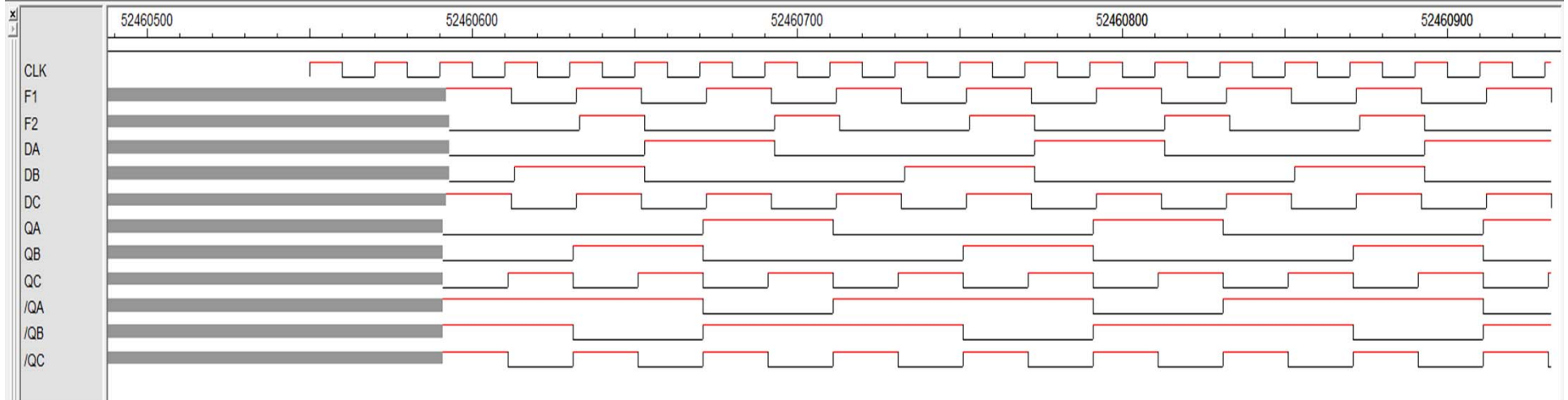
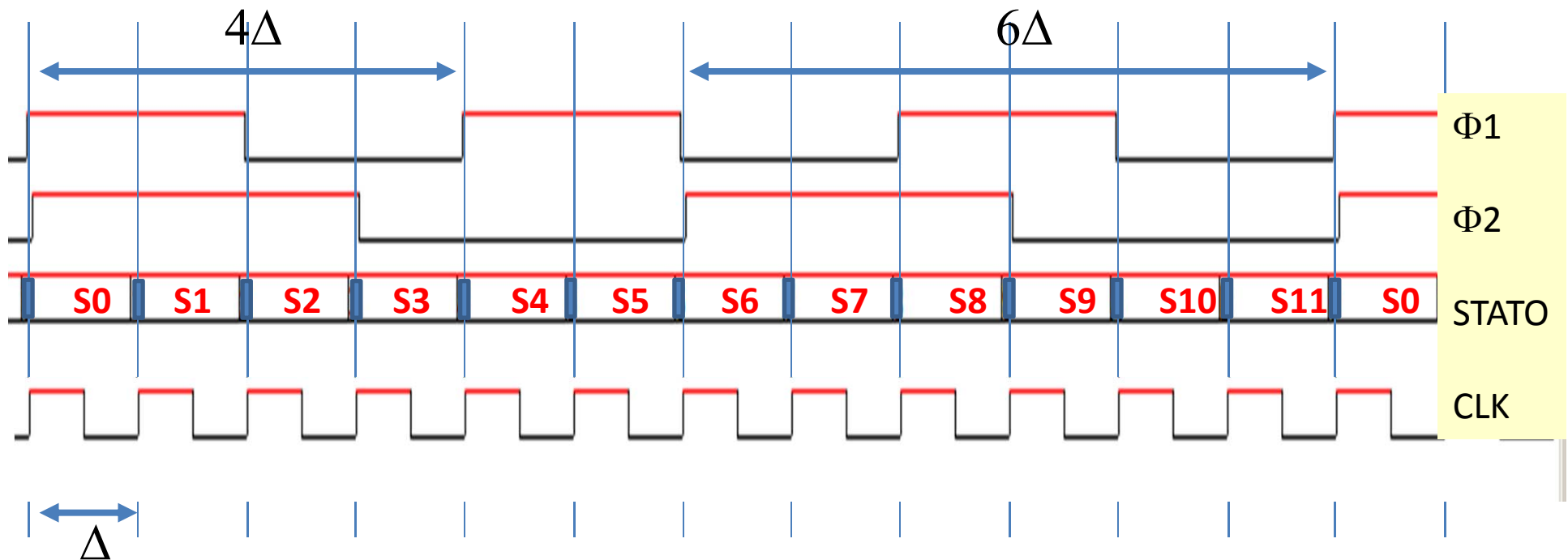
ALL LIBRARIES


Filter: or

- Glitch Detector
- MOTOR
- NOR-2
- NOR-2 (1-Inv)
- NOR-2 O.C.
- NOR-3
- NOR-4
- NOR-5
- NOR-8
- OPTO ISOLATOR
- OR-2**
- OR-2 (1-Inv)
- OR-2 (2-Inv)
- OR-3
- OR-3 (1-Inv)
- OR-3 (2-Inv)
- OR-4
- OR-5
- OR-8
- PHOTORESISTOR
- Port Bidir
- Port Bidir
- Port In
- Port In
- Port Out




 Come ottenere un duty cycle del 50% nel divisore della frequenza del clock secondo un rapporto **3:2**




FSM: # 12 STATI \leftrightarrow # 4 Flip-Flop

	@ t_n A B C D Q Q Q Q	@ t_{n+1} A B C D Q Q Q Q	@ t_n ϕ^1 ϕ^2	@ t_n A B C D Q Q Q Q
S ₀	0 0 0 0	0 0 0 1	1 1	0 0 0 1
S ₁	0 0 0 1	0 0 1 0	1 1	0 0 1 0
S ₂	0 0 1 0	0 0 1 1	0 1	0 0 1 1
S ₃	0 0 1 1	0 1 0 0	0 0	0 1 0 0
S ₄	0 1 0 0	0 1 0 1	1 0	0 1 0 1
S ₅	0 1 0 1	0 1 1 0	1 0	0 1 1 0
S ₆	0 1 1 0	0 1 1 1	0 1	0 1 1 1
S ₇	0 1 1 1	1 0 0 0	0 1	1 0 0 0
S ₈	1 0 0 0	1 0 0 1	1 1	1 0 0 1
S ₉	1 0 0 1	1 0 1 0	1 0	1 0 1 0
S ₁₀	1 0 1 0	1 0 1 1	0 0	1 0 1 1
S ₁₁	1 0 1 1	0 0 0 0	0 0	0 0 0 0
	1 1 0 0	X X X X	X X	X X X X
	1 1 0 1	X X X X	X X	X X X X
	1 1 1 0	X X X X	X X	X X X X
	1 1 1 1	X X X X	X X	X X X X

Q^AQ^B	Q^CQ^D			
Q^AQ^B	00	01	11	10
00	0	0	0	0
01	0	0	1	0
11	X	X	X	X
10	1	1	0	1

$$D^A = (\overline{A} \overline{B} C) + (A B C D) + (A \overline{B} C \overline{D})$$

Q^AQ^B	Q^CQ^D			
Q^AQ^B	00	01	11	10
00	0	0	1	0
01	1	1	0	1
11	X	X	X	X
10	0	0	0	0

$$(A \overline{B} \overline{C})$$

$$(\overline{A} \overline{B} C D)$$

$$(A B C \overline{D})$$

Q^AQ^B	Q^CQ^D			
Q^AQ^B	00	01	11	10
00	0	1	0	1
01	0	1	0	1
11	X	X	X	X
10	0	1	0	1

$$(\overline{A} \overline{B} C D)$$

$$(A \overline{B} C \overline{D})$$

Q^AQ^B	Q^CQ^D			
Q^AQ^B	00	01	11	10
00	1	0	0	1
01	1	0	0	1
11	X	X	X	X
10	1	0	0	1

$$(\overline{A} \overline{D})$$

