

8/11



$$C_1 = 1 \text{ nF}$$

$$V_{C1} = 10 \text{ V}$$

$$C_2 = 2 \text{ nF}$$

$$V_{C2} = 20 \text{ V}$$

$$Q_{\text{tot}} = Q_1 + Q_2$$

$$C_{\text{eq}} = C_1 + C_2$$

$$V_F = \frac{Q_1}{C_1} = \frac{C_1 V_1 + C_2 V_2}{C_1 + C_2}$$


$$\left[\begin{array}{l} E_1 = 50 \cdot 10^{-8} \text{ J} \\ E_2 = 4,0 \cdot 10^{-7} \text{ J} \end{array} \right] \Rightarrow E_{\text{q}} = 417 \text{ nJ}$$

$$\left. \begin{array}{l} 50 \text{ nJ} \\ 400 \text{ nJ} \end{array} \right\}$$

$$450 \text{ nJ}$$

$$-33 \text{ nJ}$$

$$-7,4\%$$

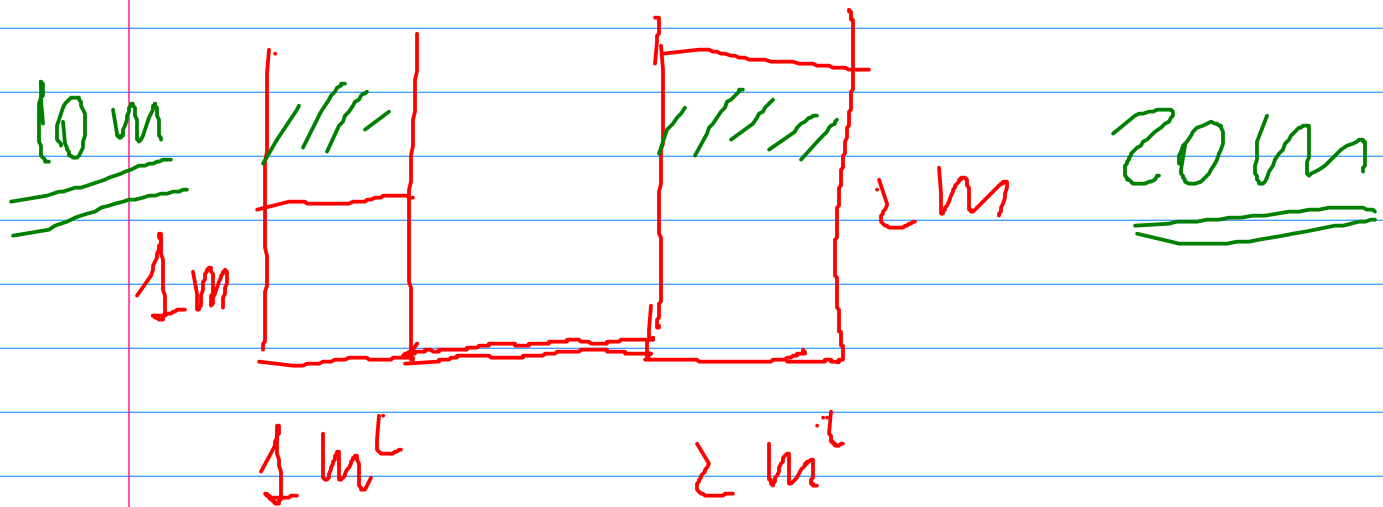

$$S_t = S_1 + S_2 \quad V_t = V_1 + V_2$$

$$h_g = \frac{V_t}{S_t} = \frac{S_1 \cdot h_1 + S_2 \cdot h_2}{S_1 + S_2}$$

$$E_1 = m_1 g h_1 / 2 = \frac{1}{2} \rho g S_1 \cdot h_1 \cdot h_1$$

$$= \frac{1}{2} \rho g S_1 h_1^2 \rightarrow \frac{1}{2} \rho v^2$$