
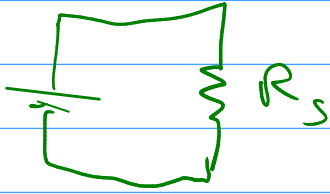


$$1) \sum_i \Delta V_i = 0$$

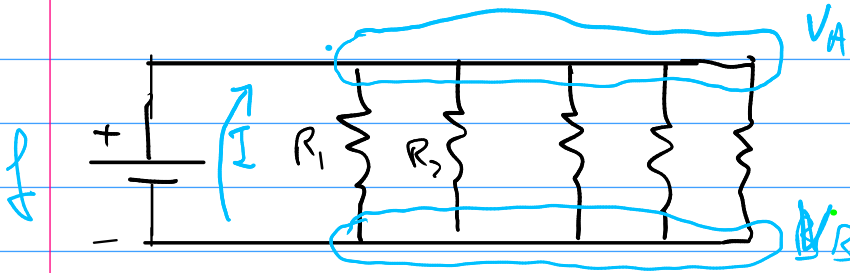" $\Delta V_i = i R_i = \frac{R_i}{\sum_i R_i} \propto R_i$ "
part. di tensione



$$R_s = \sum_i R_i \Rightarrow \text{Serie} \rightarrow \text{stesse correnti!}$$



Equipotenziali!


\rightarrow part. di corrente



$$I_{A \rightarrow B}^{(i)} = \frac{V_A - V_B}{R_i}, \dots \text{etc! etc.}$$

$$I = \sum_i I_i$$
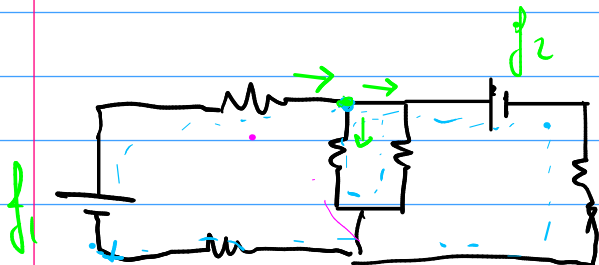
$$\Rightarrow \frac{1}{R_p} = \sum_i \frac{1}{R_i}$$




$$1) \sum_i \Delta V_i = 0$$

$$2) \sum_i I_i = 0$$

a) wert di I_i arbitrary

b) si risolvono le equazioni wrt I_i

c) segni \rightarrow versi

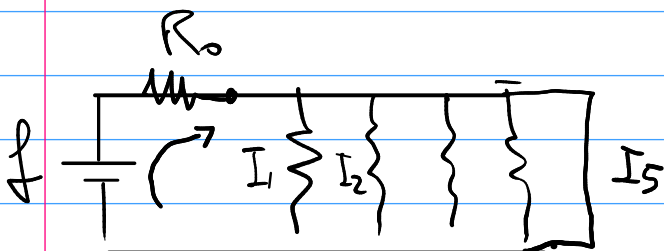


$$I_i \propto \frac{1}{R_i}$$

! ~~no is~~



$$I_0 = \mathcal{E} / R_0$$

$$I_5 = I_0$$


$$I_1 = I_2 = I_3 = I_4$$

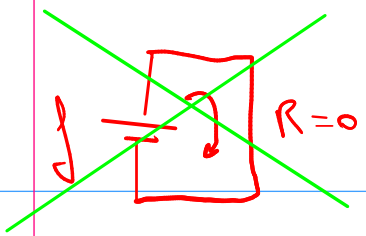

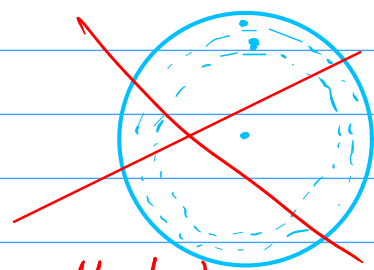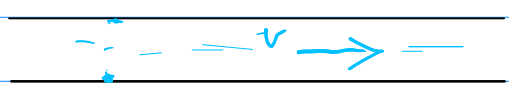
~~$$I = \frac{d}{0} \rightarrow \infty$$~~



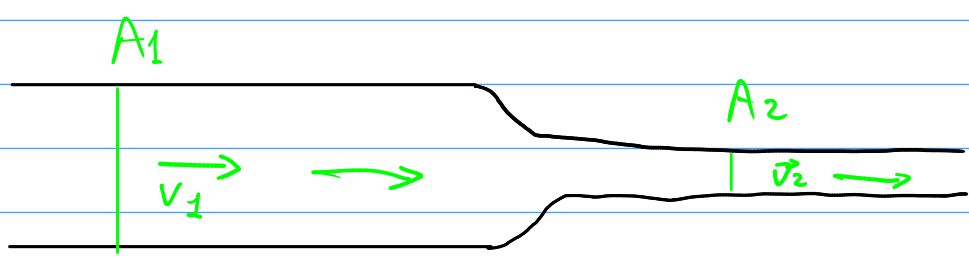- no viscositate (no atitii)
- incompresibili


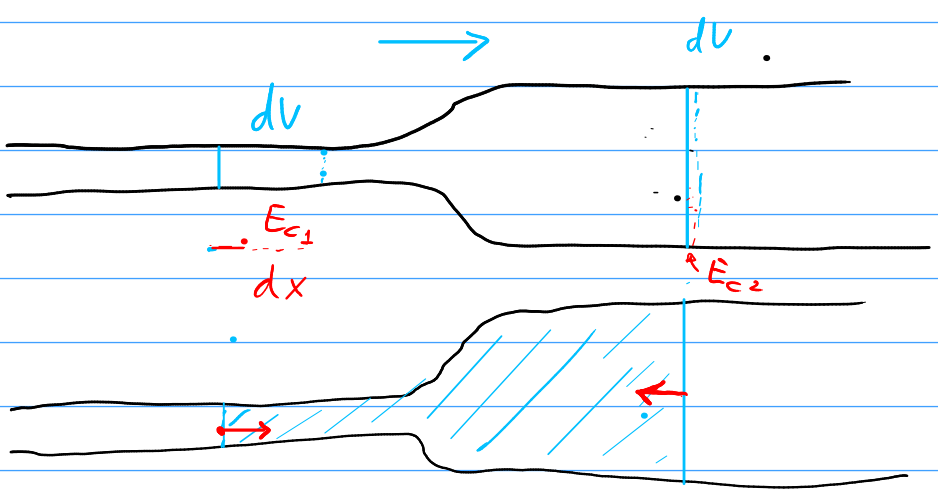
$$A_1 \cdot v_1 = A_2 v_2 \Rightarrow A_i \cdot v_i = \text{constant}$$



$$e = \rho v^2$$

$$L_1 > 0$$

$$L_2 < 0$$

$$L_{tot} = L_1 + L_2 = \Delta E_c$$

